

# Electrical Oscillations in an L-C Circuit

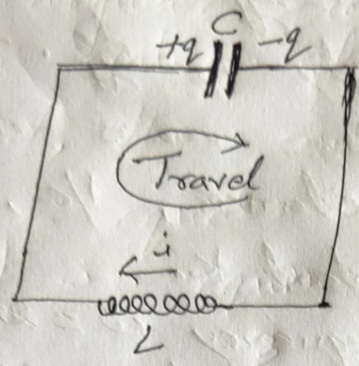


Fig ①

Fig ① → Applying Kirchoff's loop rule to the L-C circuit. The direction of travel around the loop in the loop equation is shown. Starting at the lower-right corner of the circuit and adding voltages as we go clockwise around the loop then we get

$$-L \frac{di}{dt} - \frac{q}{C} = 0 \quad \text{--- ①}$$

$$\therefore i = \frac{dq}{dt}, \therefore \frac{di}{dt} = \frac{d^2q}{dt^2}$$

putting this in equ<sup>n</sup> ① and divide by  $-L$  to obtain

$$\frac{d^2q}{dt^2} + \frac{1}{LC} q = 0 \quad \text{--- ②}$$

But in simple harmonic motion

$$\frac{d^2x}{dt^2} = -\left(\frac{k}{m}\right)x \quad \text{or}$$

$$\frac{d^2x}{dt^2} + \frac{k}{m} x = 0$$

In an L-C circuit the capacitor charge  $q$  plays the role of the displacement  $x$ , and the current  $i = \frac{dq}{dt}$  is analogous to the particle's velocity  $v_x = \frac{dx}{dt}$ . The inductance  $L$  is analogous to the mass  $m$ , and the reciprocal of capacitance,  $1/c$ , is analogous to the force constant  $k$ .

The angular frequency  $\omega = 2\pi f$  of the harmonic oscillator is equal to  $(k/m)^{1/2}$  and the position is given a function of time like

$$x = A \cos(\omega t + \phi)$$

where the amplitude  $A$  and the phase angle  $\phi$  depend on the initial conditions. In the analogous electrical situation the capacitor charge  $q$  is given by

$$q = Q \cos(\omega t + \phi) \quad \text{--- (3)}$$

and the angular frequency  $\omega$  of oscillation is given by

$$\omega = \sqrt{\frac{1}{LC}} \quad \text{--- (4)}$$

$\omega$  = Angular frequency of oscillation in an L-C circuit.

$L$  = Inductance

$C$  = Capacitance

then 
$$i = -\omega Q (\sin \omega t + \phi) \quad \text{--- (5)}$$

[From eqn (3) & (4)]  
where  $\frac{dq}{dt} = i$

Thus the charge & current in an L-C circuit oscillate sinusoidally with time with an angular frequency determined by the values of L and C. The ordinary frequency  $f$ , the number of cycles per second, is equal to  $\omega/2\pi$ . The constants  $Q$  and  $\phi$  in eqn (3) and eqn (5) are determined by the initial conditions. If at time

$t=0$  the left-hand capacitor plate in fig (1) has its maximum charge  $Q$  and the current  $i$  is zero, then  $\phi=0$ . If  $q=0$  at  $t=0$ , then  $\phi = \pm \pi/2$  rad.

— X —