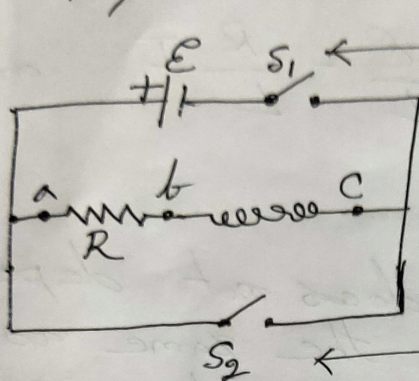


# L-R Circuit and Current Growth in page-1 in an L-R Circuit

A circuit that includes both a resistor and an inductor, and possibly a source of emf, is called an R-L circuit.



closing  $S_1$  connects the R-L combination in series with a source of emf  $E$ .

closing switch  $S_2$  while opening switch  $S_1$  disconnects the combination from the source.

Fig 1: An R-L Circuit

Let  $i$  be the current at some time  $t$  after switch  $S_1$  is closed and let  $di/dt$  be its rate of change at that time. The potential differences  $V_{ab}$  across the resistor and  $V_{bc}$  across the inductor are

$$V_{ab} = iR \quad \text{and} \quad V_{bc} = L \frac{di}{dt}$$

then according to Kirchhoff's loop rule.

$$E - iR - L \frac{di}{dt} = 0 \quad \text{--- (1)}$$

Solving this for  $\frac{di}{dt}$ , we find that the rate of increase of current is

$$\frac{di}{dt} = \frac{E - iR}{L} = \frac{E}{L} - \frac{R}{L} i \quad \text{--- (2)}$$



If switch  $S_1$  is 1st closed,  $i = 0$  page: 21  
 drop across  $R$  is zero. potential

The initial rate of change of current is  $\left(\frac{di}{dt}\right)_{\text{initial}} = \frac{\mathcal{E}}{L}$



The greater the inductance  $L$ , the more slowly the current increases.

$$\left(\frac{di}{dt}\right)_{\text{final}} = 0 = \frac{\mathcal{E}}{L} - \frac{R}{L} I \quad \text{and}$$

$$I = \frac{\mathcal{E}}{R}$$

The final current  $I$  does not depend on the inductance  $L$ . It is the same as it would be if the resistance  $R$  alone were connected to the source with emf  $\mathcal{E}$ .

Switch  $S_1$  is closed at  $t = 0$

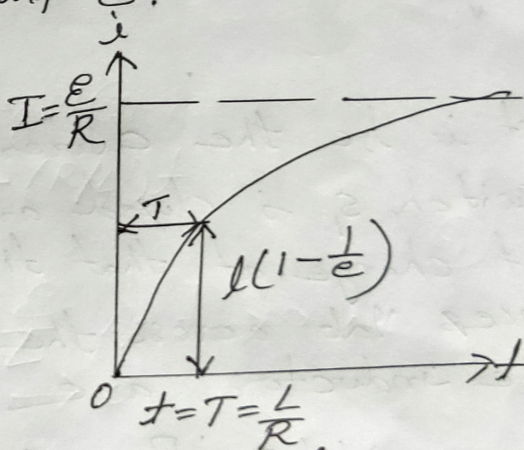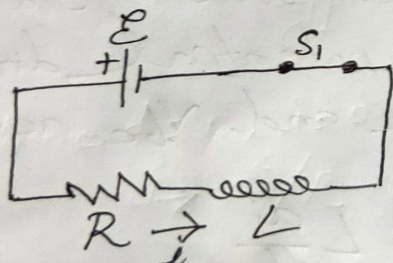

Graph of  $i$  versus  $t$  for growth of current in an  $R$ - $L$  circuit with an emf in series. The final current  $I = \mathcal{E}/R$ ; after one time constant  $T$ , the current is  $1 - \frac{1}{e}$  of this value.

Fig 2 :- Behavior of the current as a function of time



After Rearranging eqn<sup>n</sup> (2) we have Page:-3

$$\frac{di}{i - (E/R)} = -\frac{R}{L} dt$$

$$\int_0^i \frac{di'}{i' - (E/R)} = - \int_0^t \frac{R}{L} dt'$$

$$\ln \left( \frac{i - (E/R)}{-E/R} \right) = -\frac{R}{L} t$$

Now we take exponentials of both sides and solve for  $i$ .

$$i = \frac{E}{R} \left( 1 - e^{-(R/L)t} \right) \quad \text{--- (3)}$$

where  $i$  = current in an R-L circuit with emf.

Taking the derivative of eqn<sup>n</sup> (3) we have

$$\frac{di}{dt} = \frac{E}{L} e^{-(R/L)t} \quad \text{--- (4)}$$

At time  $t=0$ ,  $i=0$  and  $\frac{di}{dt} = \frac{E}{L}$  As  $t \rightarrow \infty$ ,  
 $i \rightarrow E/R$  and  $\frac{di}{dt} \rightarrow 0$

$$\text{Time constant } \tau = \frac{L}{R} \quad \left[ \begin{array}{l} \text{where } L = \text{Inductance} \\ R = \text{Resistance} \end{array} \right] \quad \text{--- (5)}$$

----- X -----