

> Date


Mon Tue Wed Thu Fri Sat Sun

Degree - II, Paper - IV, Group - B, 15/02/2024

Name: Gureedhar Kumar

Topic: Growth of charge - LCR.

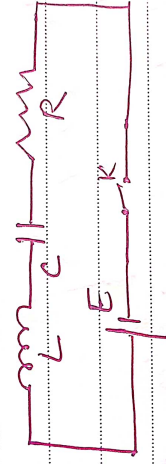In this circuit, when 'K' switch is pressed, the capacitor is charged. Let 'Q' be the charge on capacitor and I is the current in the circuit at an instant 't' during charging.



potential difference across the

$$\text{Capacitor} = \frac{Q}{C}$$

* Potential difference across the inductance,
 $= L \frac{dI}{dt}$

* Potential difference across the resistor
 $= IR$

Adding up all the potential difference

$$L \frac{dI}{dt} + RI + \frac{Q}{C} = E \quad \text{--- (1)}$$

$$I = \frac{dQ}{dt} \rightarrow L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = E$$

Degree - II, paper - IV, Group B, 15/02/2017
Name: - Gurdeepan Kumar

$$\Rightarrow \frac{d^2\theta}{dt^2} + \frac{R}{L} \frac{d\theta}{dt} + \frac{\theta - CE}{LC} = 0$$

Let us substitute $\frac{R}{L} = 2b$ and $\frac{1}{LC} = k^2$

$$\frac{d^2\theta}{dt^2} + 2b \frac{d\theta}{dt} + k^2(\theta - CE) = 0 \quad \text{--- (2)}$$

Let $x = \theta - CE$, then,

$$\frac{d^2x}{dt^2} + 2b \frac{dx}{dt} + k^2x = 0 \quad \text{--- (3)}$$

Hence, the most general solution of eqn (3)

$$x = A e^{(-b + \sqrt{b^2 - k^2})t} + B e^{(-b - \sqrt{b^2 - k^2})t}$$

We can consider $CE = \theta_0 =$ Final steady charge on the capacitor

$$\therefore x = \theta - CE = \theta - \theta_0$$

$$\therefore \theta - \theta_0 = A e^{(-b + \sqrt{b^2 - k^2})t} + B e^{(-b - \sqrt{b^2 - k^2})t}$$

$$\Rightarrow \theta = \theta_0 + A e^{(-b + \sqrt{b^2 - k^2})t} + B e^{(-b - \sqrt{b^2 - k^2})t}$$

> Date

Degree - II, paper - IV, Group - B, 15/02/2019
 using initial condition; Name: Gurukulka
 at, $t=0$, $\phi=0$

$$\therefore 0 = \phi_0 + (A+B)$$

$$\text{or } \boxed{A+B = -\phi_0} \quad \text{--- (5)}$$

By differentiating eqn (4) w.r.t time (t)

$$\frac{d\phi}{dt} = 0 + A(-b + \sqrt{b^2 - k^2})e + B(-b - \sqrt{b^2 - k^2})e^{(b + \sqrt{b^2 - k^2})t}$$

$$\text{at } t=0, \quad \frac{d\phi}{dt} = 0$$

$$0 = A(-b + \sqrt{b^2 - k^2}) + B(-b - \sqrt{b^2 - k^2})$$

$$0 = -bA + A\sqrt{b^2 - k^2} - bB - B\sqrt{b^2 - k^2}$$

$$b(A+B) = \sqrt{b^2 - k^2}(A-B)$$

from eqn (5)

$$-\phi_0 b = A - B \quad \text{--- (6)}$$

Adding eqn (5) and (6)

$$2A = \frac{-\phi_0(b + \sqrt{b^2 - k^2})}{\sqrt{b^2 - k^2}}$$

> Date

Mon Tue Wed Thu Fri Sat Sun

Degree - II, Paper - IV, Group - B, 15/07/2014

$$\Rightarrow A = -\frac{1}{2} \phi_0 \frac{1+b}{\sqrt{b^2-k^2}}$$


Circuit ka Km

$$\Rightarrow A = -\frac{1}{2} \phi_0 \left(1 + \frac{b}{\sqrt{b^2-k^2}} \right) \quad \text{--- (7)}$$

$$B = -\frac{1}{2} \phi_0 \left(1 - \frac{b}{\sqrt{b^2-k^2}} \right) \quad \text{--- (8)}$$

Now substituting the value of A and B in Eqn (4) we get
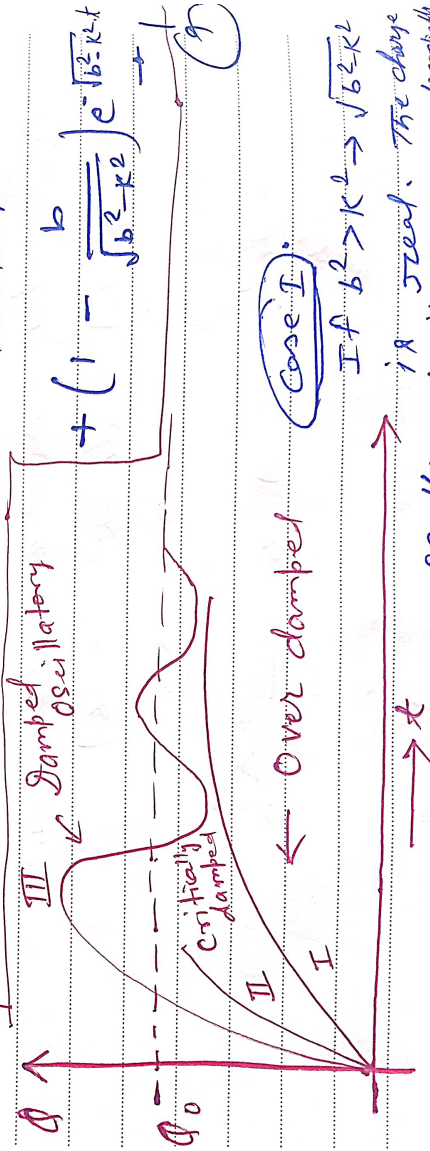
$$\phi = \phi_0 - \frac{1}{2} \phi_0 e^{-bt} \left[\left(1 + \frac{b}{\sqrt{b^2-k^2}} \right) e^{\sqrt{b^2-k^2}t} + \left(1 - \frac{b}{\sqrt{b^2-k^2}} \right) e^{-\sqrt{b^2-k^2}t} \right]$$



If $b^2 > k^2 \rightarrow \sqrt{b^2-k^2}$ is real. The charge on the capacitor grows exponentially with time and attains the maximum value ϕ_0 asymptotically. The charge is known as "Over dead beat".

Degree - II paper - IV Group - B, 15/04/2024

Case II

If $b^2 = k^2$, the charge rises to the maximum value q_0 in a short time. Such an charge is called critically damped.

Case III

If $b^2 < k^2 \rightarrow \sqrt{b^2 - k^2}$ is imaginary
Let $\sqrt{b^2 - k^2} = i\omega$ where $i = \sqrt{-1}$ and
 $\omega = \sqrt{k^2 - b^2}$

Then eqn (9) can be written as

$$Q = q_0 - \frac{1}{2} q_0 e^{-bt} \left[\left(1 + \frac{b}{i\omega}\right) e^{i\omega t} + \left(1 - \frac{b}{i\omega}\right) e^{-i\omega t} \right]$$

$$Q = q_0 - q_0 \cdot e^{-bt} \left[\frac{e^{i\omega t} + e^{-i\omega t}}{2} + \frac{b}{\omega} \left(\frac{e^{i\omega t} - e^{-i\omega t}}{2i} \right) \right]$$

$$Q = q_0 - q_0 \cdot e^{-bt} \left[\cos \omega t + \frac{b}{\omega} \sin \omega t \right]$$

$$Q = q_0 \left[1 - \frac{e^{-bt}}{\omega} (\omega \cos \omega t + b \sin \omega t) \right]$$

Let $\omega = k \sin \alpha$ and $b = k \cos \alpha$

$$\therefore \text{form of } = \frac{\omega}{b}$$

$$Q = q_0 \left[1 - \frac{e^{-bt}}{\omega} (K \sin \alpha \cos \omega t + K \cos \alpha \sin \omega t) \right]$$

degree-II, paper-IV, Group-B, 15/07/2014

$$q = q_0 \left[1 - \frac{ke^{-bt}}{\omega} \sin(\omega t + k) \right] \quad (10)$$

In the begining, we considered,

$$k = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \quad \text{and} \quad b = \frac{R}{2L}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$q = q_0 \left[1 - \frac{e^{-\frac{R}{2L}t} \sqrt{\frac{1}{LC}}}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}} \sin \left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} t + \alpha \right) \right]$$

This eqn represents a damped oscillatory charge as shown by the curve III. The charge oscillates above and below q_0 till it finally settles down to q_0 value. The frequency of oscillation in the circuit is given by

$$f = \frac{\omega}{2\pi} = \frac{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$\text{Where } R=0 \rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$