

2008 MAY


Degree-II, Paper-IV Group-B,
Date: 20/02/2024

21
WED

Name:- Giridhar Kumar.

Topic:- Anderson's Bridge.

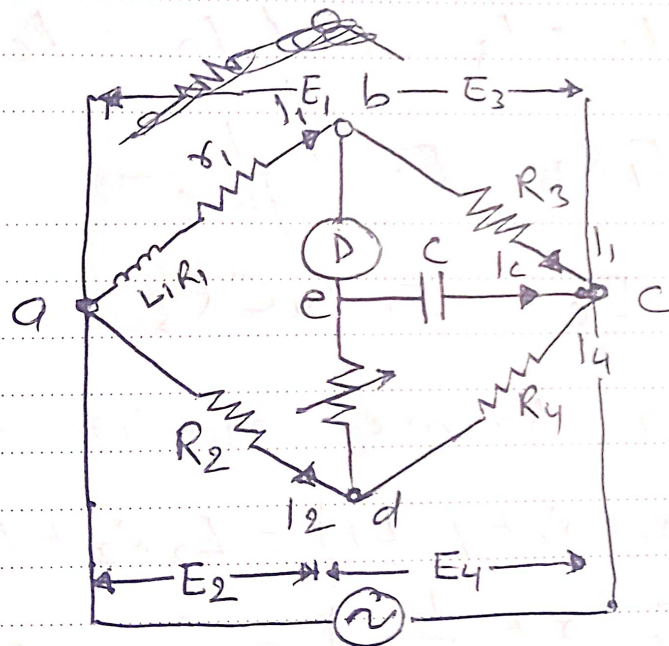The Anderson's bridge gives the accurate measurement of self-inductance of the circuit. The bridge is the advanced form of Maxwell's inductance capacitance bridge.



22
THU

Construction of Anderson's Bridge:-

The bridge has four arms ab, bc, cd and ad. The arm ab consists unknown inductance along with the resistance. And other three arms consist the

23
FRI

Degree-II, paper-IV, Group-B
purely resistive arms connected in series with the circuit.

Theory of Anderson Bridge:-

Let L_1 - unknown inductance having a resistance R_1 . R_2 , R_3 and R_4 - known non-inductive resistance C_4 - standard capacitor

At balance condition

$$I_1 = I_3 \text{ and } I_2 = I_c + I_4$$

Now
$$I_1 R_3 = I_c \times \frac{1}{j\omega C}$$

$$I_c = I_1 \omega C R_3$$

The other balance condition eqn.

$$I_1 (\gamma_1 + R_1 + j\omega L_1) = I_2 R_2 + I_c \gamma$$

$$I_c \left(\gamma + \frac{1}{j\omega C} \right) = (I_2 - I_c) R_4$$

By substituting the value of I_c in the above eqn.

$$I_1 (\gamma_1 + R_1 + j\omega L_1) = I_2 R_2 + I_1 j\omega C R_3 \gamma$$

$$I_1 (\gamma_1 + R_1 + j\omega L_1 - j\omega C R_3 \gamma) = I_2 R_2$$

2008 MAY

25
SUN

Degree-II, paper-IV, Group-B.

$$I_1(R_3 + j\omega R_3 R_4 + j\omega C R_3 r) = I_2 R_4$$

on equating the equation, we get

$$I_1(r_1 + R_1 + j\omega L_1 - j\omega C R_3 r) = I_2 \left(\frac{R_2 R_2}{R_3} + \frac{j\omega C R_3 r R_2}{R_4} + j\omega C R_3 R_2 \right)$$

Now

$$R_1 = \frac{R_1 R_3}{R_4} - r_1$$

And

$$L_1 = C \frac{R_3}{R_4} [4(R_4 + R_2) + R_2 R_4]$$

26
MON

Notes

| 2008 | Sun | Mon | Tue | Wed | Thu | Fri | Sat |
|------|-----|-----|-----|-----|-----|-----|-----|
| | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| | 8 | 9 | 10 | 11 | 12 | 13 | 14 |